


Classical bits, gates, and circuits

classical bit $\hat{=}$ classical 2-state system:



$$X \in \{0, 1\} = \mathbb{Z}_2$$

n-bit register :

 

State :

$$X = (X_{n-1}, X_{n-2}, \dots, X_0) \in \mathbb{Z}_2^n$$

n bit binary number :

$$00 \dots 00 = 0$$

$$00 \dots 01 = 1$$


$$00 \dots 10 = 2$$

$$00 \dots 11 = 3$$

$$\vdots$$
$$11 \dots 11 = 2^n - 1$$

$$\rightarrow \mathbb{Z}_2^n \hat{=} \{0, 1, 2, \dots, 2^n - 1\}$$


Logic gate:


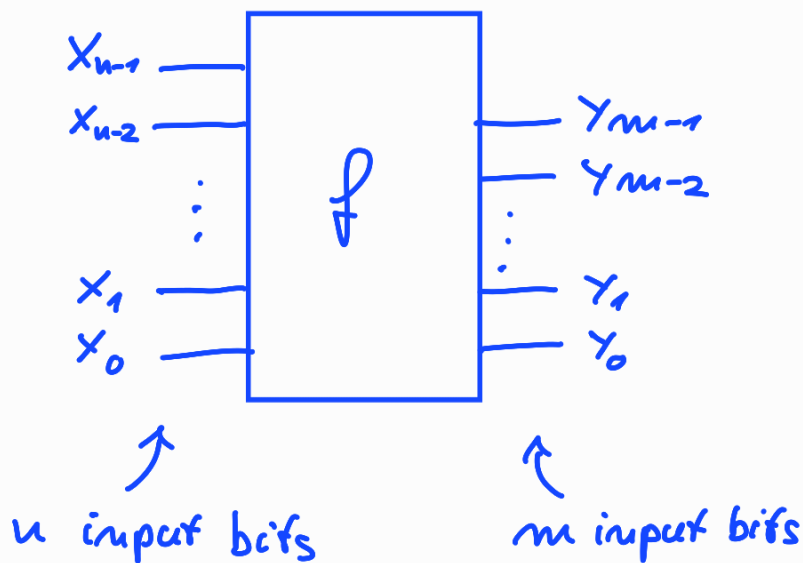


implements m -valued boolean function:

$$f: \mathbb{Z}_2^u \rightarrow \mathbb{Z}_2^m$$
$$x \mapsto y = f(x)$$

Elementary gates:

 


  


circuit = directed, acyclic graph

edge $\hat{=}$ wire

node $\hat{=}$ gate

 

e. g. half-adder circuit :

 


Thm. : Every boolean function $f: \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^m$ can be implemented by a circuit made of NAND and BRANCH gates only : $\{ \text{NAND}, \text{BRANCH} \}$ is a universal set of logic gates .

 Examples :





we prove Thm. by induction,
w. l. o. g. $n = 1$.



$n \rightarrow n+1$:


$$f : \mathbb{Z}_2^{\underline{n+1}} \rightarrow \mathbb{Z}_2$$

$$\rightarrow f_0, f_1 : \mathbb{Z}_2^{\underline{n}} \rightarrow \mathbb{Z}_2 \text{ def. by}$$

$$f_{\underline{0}}(x_1, \dots, x_n) = f(\underline{0}, x_1, \dots, x_n)$$

$$f_{\underline{1}}(x_1, \dots, x_n) = f(\underline{1}, x_1, \dots, x_n)$$

 by inductive hypothesis f_0 and f_1
can be implemented with NAND and
BRANCH; and so f :



↑
circuit for f !

□


circuit model of computation:

computation



circuit
 
$$f: \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^m$$



→ computational cost of comp. f:

$r(f)$ = number of NAND
and BRANCH needed
to build circuit C_f

• emulation of C_f on CPU-computer

requires

$$r' = \text{poly}(r(f))$$

CPU - operations !

- CPU - computer key of $r'(f)$
CPU - operations (to compute f) can
be implemented in a circuit
with

$$r = \text{poly}(r'(f))$$

NAND & BRANCH gates !

→ circuits and CPU - computers are
polynomially equivalent !



Reversible Computation

Circuits made of irreversible gates
(as AND, OR, XOR, NAND, ...) makes
computation an irreversible process!


→ energy dissipation (1960!)

→ incompatible with unitary and
thus reversible dynamics of a
quantum system ("computer")
(1990!)


fortunately, there exist universal
reversible gates → reversible computation!

1) CSWAP : controlled swap

(Fredkin-gate)

 


$c = 0$:

 

no
swap!



$c = 1$:

 

swap!

obviously reversible and also


universal:

  

→ NAND, BRANCH : universality!

another universal + reversible gate:

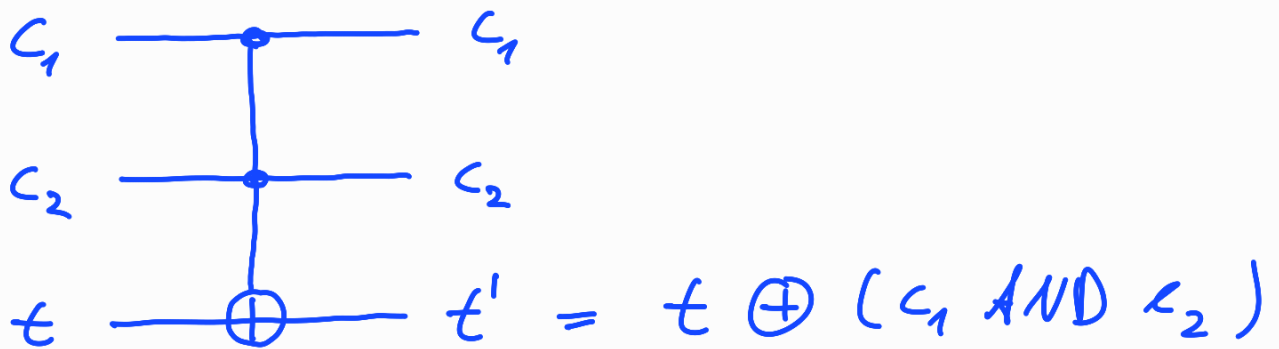2) CCNOT : doubly controlled NOT
(Toffoli-gate)



(universality: problem 6. on sheet 2)

Conclusion:

by use of reversible, universal gates
any computation can be done reversibly,
- without dissipating energy!

reversible computation of non-injective

(= irreversible) function $f: \mathbb{Z}_2^u \rightarrow \mathbb{Z}_2^m$?!

→ switch to injective (= reversible)

function $\tilde{f}: \mathbb{Z}_2^{u+m} \rightarrow \mathbb{Z}_2^{u+m}$

def. by

$$\tilde{f}(x, y) = (x, y \oplus f(x)) !$$

• reversible :

$$\tilde{f} \circ \tilde{f}(x, y) = \tilde{f}(x, y \oplus f(x))$$

$$= (x, y \oplus \underbrace{f(x) \oplus f(x)}_{=0})$$

$$= (x, y)$$

$$\rightarrow \tilde{f} = \tilde{f}^{-1}$$

• on input $(x, 0)$:

$$\tilde{f}(x, 0) = (x, \underline{f(x)})$$

